



ASSIGNMENT 5 (EXTRA)

Abdalrahman Ali Eltaher

Q [1]

Type of errors:

- 1- Multiple drivers on out1
- 2- Possible division by zero
- 3- Bit-width mismatch between ns and in1
- 4- r1 is unused
- 5- Inconsistent reset logic
- 6- Use of 1'bx in synthesis

Q [2]

Code:

```
1  module detect_010(X,clk,rst,Y,count);
2
3  parameter IDLE =2'b00 ;
4  parameter ZERO = 2'b01 ;
5  parameter ONE = 2'b10 ;
6  parameter STORE = 2'b11 ;
7
8  input X,clk,rst;
9
10 output reg Y;
11 output reg [9:0] count;
12
13 //current state (cs) and next state(ns)
14 reg [1:0] cs , ns;
15
16 //next state
17 always @(*) begin
18     case (cs)
19         IDLE:
20             begin
21                 if(X)
22                     ns = IDLE;
23                 else
24                     ns = ZERO;
25             end
26         ZERO:
27             begin
28                 if(X)
29                     ns = ONE;
30                 else
31                     ns = ZERO;
32             end
33         ONE:
34             begin
35                 if(X)
36                     ns = IDLE;
37                 else
38                     ns = STORE;
39             end
40         STORE:
41             begin
42                 if(X)
43                     ns = IDLE;
44                 else
45                     ns = ZERO;
46             end
47         default: ns = IDLE ;
48     endcase
49 end
50
51 // state memory
52 always @(posedge clk or posedge rst ) begin
53     if(rst)
54         cs <= IDLE;
55     else
56         cs <= ns ;
57 end
58
59 // output logic
60 always @(posedge clk or posedge rst ) begin
61     if (rst)begin
62         count <= 0;
63         Y <= 0;
64     end
65     else begin
66         case (cs)
67             IDLE : Y <= 0 ;
68             ZERO : Y <= 0 ;
69             ONE : Y <= 0 ;
70             STORE :
71                 begin
72                     Y <= 1 ;
73                     count <= count+1;
74                 end
75         endcase
76     end
77 end
78 endmodule
79
```


Testbench:

```

1  module detect_010_tb();
2
3  reg X_tb,clk_tb,rst_tb;
4
5  wire Y_dut;
6  wire [9:0] count_dut;
7
8  detect_010 dut(X_tb,clk_tb,rst_tb,Y_dut,count_dut);
9
10 //clock generation.
11 initial begin
12     clk_tb=0;
13     forever
14         #1 clk_tb = ~ clk_tb;
15 end
16 initial begin
17     //reset
18     rst_tb = 1 ;
19     @(negedge clk_tb);
20     rst_tb = 0 ;
21     //x = 0
22     repeat(100)begin
23         X_tb = $random;
24         @(negedge clk_tb);
25     end
26     $stop;
27 end
28 endmodule

```

Wave:

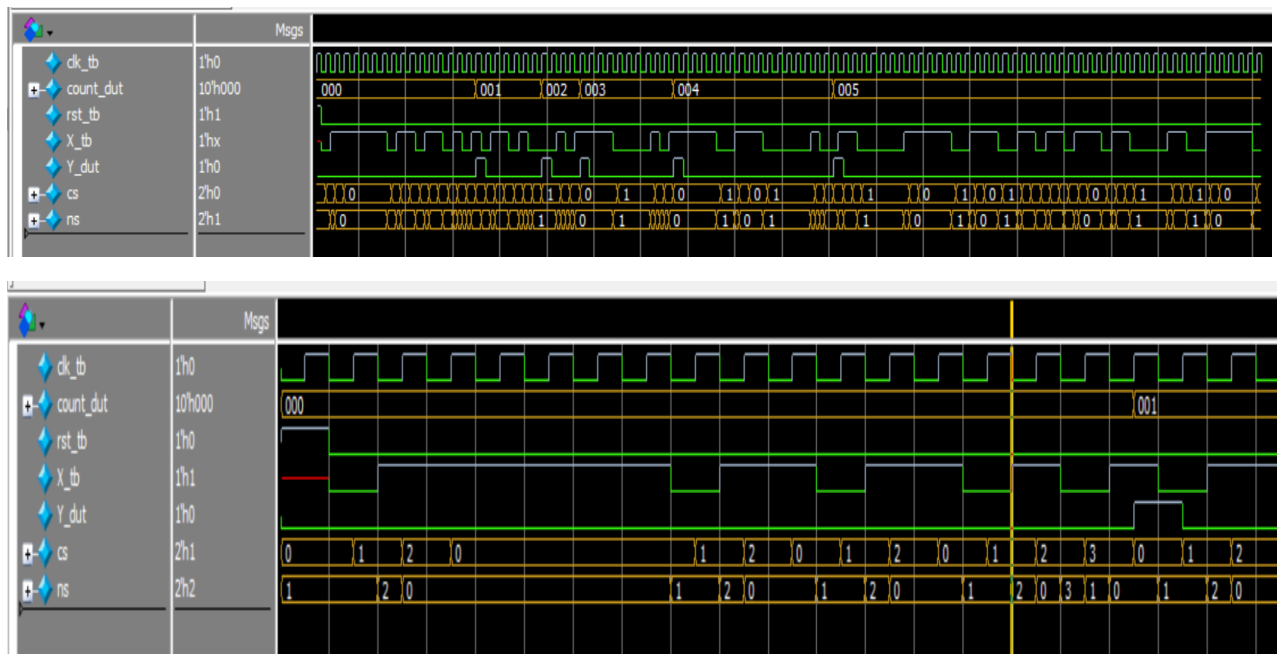

Q [3]


Code:

```
1  module seq_detector(clk,rst,in,y);
2
3      parameter S0 = 2'b00 ;
4      parameter S1 = 2'b01 ;
5      parameter S2 = 2'b10 ;
6      parameter S3 = 2'b11 ;
7
8      input clk,rst,in;
9
10     output y;
11
12     //current state (cs) and next state (ns)
13     reg [1:0] cs,ns;
14
15     //next state
16     always @(*) begin
17         case (cs)
18             S0:
19                 begin
20                     if(in)
21                         ns = S1;
22                     else
23                         ns = S0;
24                 end
25             S1:
26                 begin
27                     if(in)
28                         ns = S2;
29                     else
30                         ns = S1;
31                 end
32             S2:
33                 begin
34                     if(in)
35                         ns = S3;
36                     else
37                         ns = S2;
38                 end
39             S3:
40                 begin
41                     if(in)
42                         ns = S1;
43                     else
44                         ns = S0;
45                 end
46             default: ns =S0;
47         endcase
48     end
49
50     //state memory.
51     always @(posedge clk or posedge rst) begin
52         if(rst)
53             cs<=S0;
54         else
55             cs<=ns;
56     end
57
58     //output logic.
59     assign y = (cs ==S2 && in )? 1:0;
60
61 endmodule
62
```

Testbench:

```
1  module seq_detector_tb();
2
3  reg clk_tb,rst_tb,in_tb;
4  wire y_dut;
5  seq_detector dut (clk_tb,rst_tb,in_tb,y_dut);
6  //generate clock
7  initial begin
8      clk_tb=0;
9      forever
10         #1 clk_tb=~clk_tb;
11  end
12  initial begin
13      rst_tb = 1;
14      @(negedge clk_tb);
15      rst_tb = 0 ;
16      repeat (100)begin
17          in_tb = $random;
18          @(negedge clk_tb);
19      end
20      $stop;
21  end
22  endmodule
```


Wave:

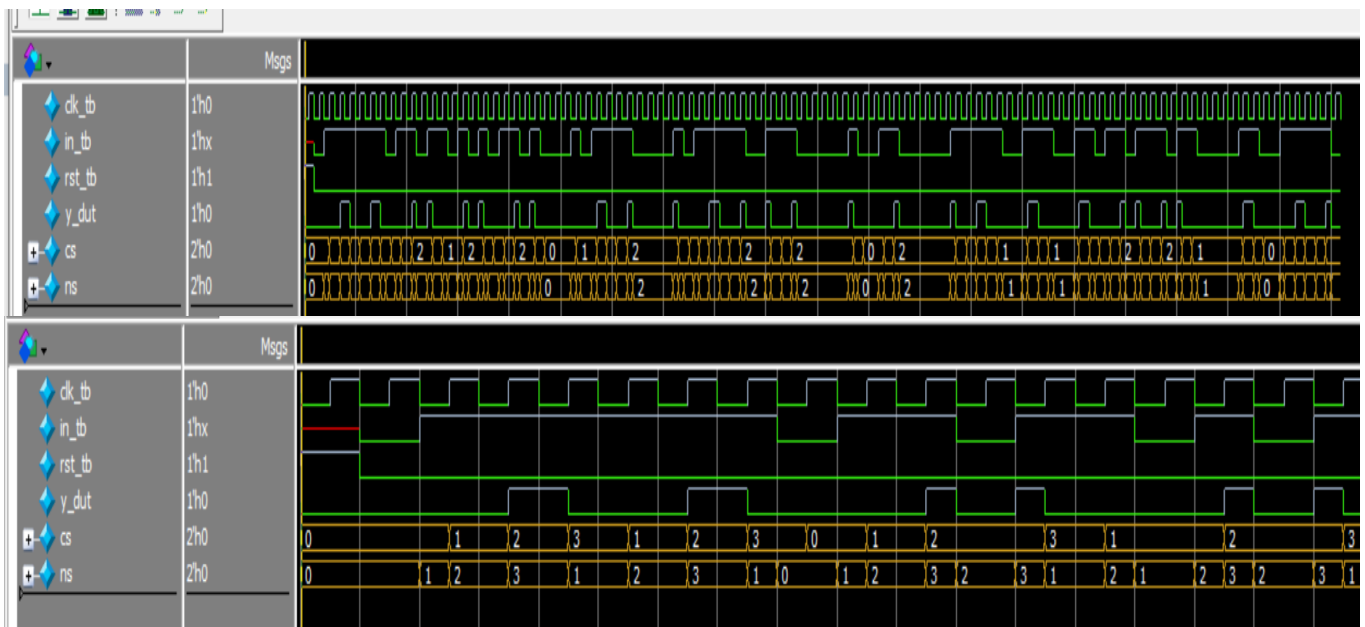

Linting snippet free from warnings or errors:

Lint Checks								
Filter: Type here								
Total : 2 Selected : 0								
Severity	status	Check	Alias	Message	Module	Category	State	Owner
		async_reset_active_...		Asynchronous reset is active high. Reset rst...	seq_detector	Clock	open	unass... 2.3.6.2
		multi_ports_in_singl...		Multiple ports are declared in one line. Mod...	seq_detector	Rtl Design ...	open	unass... 3.5.6.3

 
Snippets from the schematic after the elaboration:




Snippets from the message after the elaboration:

- ✓ Vivado Commands (4 infos, 4 status messages)
 - ✓ General Messages (4 infos, 4 status messages)
 - [IP_Flow 19-234] Refreshing IP repositories
 - [IP_Flow 19-1704] No user IP repositories specified
 - [IP_Flow 19-2313] Loaded Vivado IP repository 'C:/Xilinx/Vivado/2018.2/data/ip'.
 - [filemgmt 20-348] Importing the appropriate files for fileset: 'sources_1'
 - > [Command: synth_design -rtl -name rtl_1 (3 more like this)]
 - ✓ Elaborated Design (7 infos, 7 status messages)
 - ✓ General Messages (7 infos, 7 status messages)
 - [Synth 8-6157] synthesizing module 'seq_detector' [Q3_code.v:1]
 - [Synth 8-226] default block is never used [Q3_code.v:17]
 - [Synth 8-6155] done synthesizing module 'seq_detector' (1#1) [Q3_code.v:1]
 - [Device 21-403] Loading part xc7a35ticipg236-1L
 - [Project 1-570] Preparing netlist for logic optimization
 - > [Processing XDC Constraints (6 more like this)]
 - [Opt 31-138] Pushed 0 inverter(s) to 0 load pin(s).
 - [Project 1-111] Unisim Transformation Summary:
No Unisim elements were transformed.

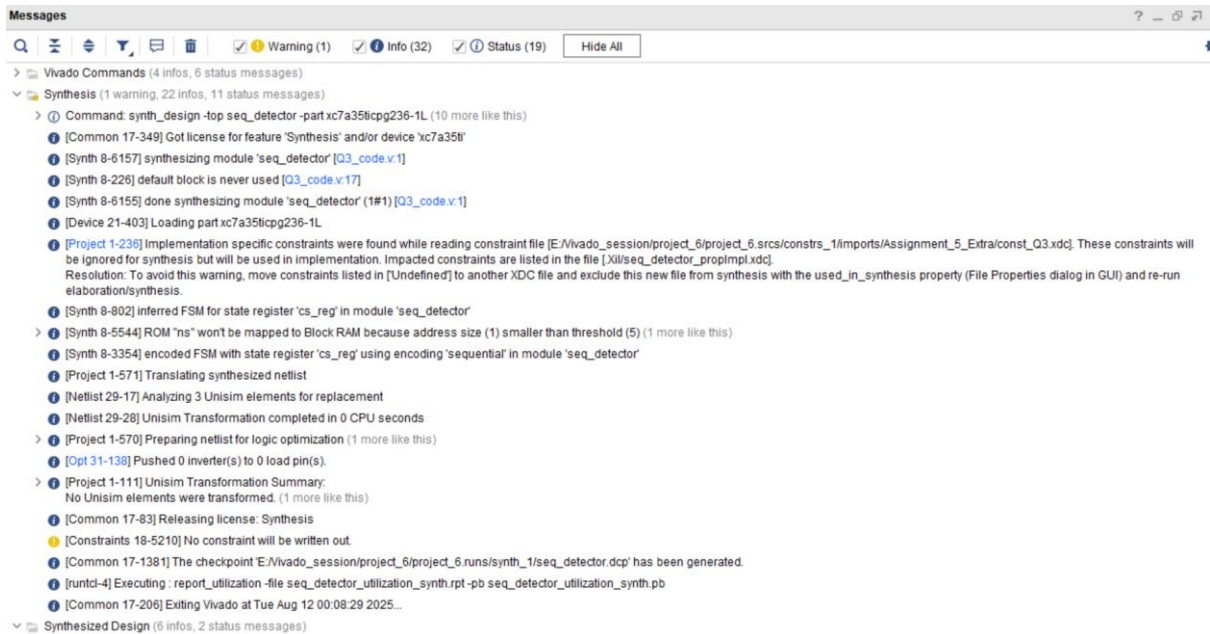Snippets from the message after the synthesis:



 Snippets from the schematic after the synthesis:



Snippets from the utilization after the synthesis:

Name	Slice LUTs (20800)	Slice Registers (41600)	Bonded IOB (106)	BUFGCTRL (32)
seq_detector	3	2	4	1

Snippets from the timing after the synthesis:

Design Timing Summary			
Setup	Hold	Pulse Width	
Worst Negative Slack (WNS): 8.339 ns	Worst Hold Slack (WHS): 0.142 ns	Worst Pulse Width Slack (WPWS): 4.500 ns	
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns	
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	
Total Number of Endpoints: 2	Total Number of Endpoints: 2	Total Number of Endpoints: 3	
All user specified timing constraints are met.			

Constraint file

```
1  ## Clock signal
2  set_property -dict { PACKAGE_PIN W5    IOSTANDARD LVCMOS33 } [get_ports clk]
3  create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk]
4  ## Switches
5  set_property -dict { PACKAGE_PIN V17    IOSTANDARD LVCMOS33 } [get_ports in]
6
7  ## LEDs
8  set_property -dict { PACKAGE_PIN U16    IOSTANDARD LVCMOS33 } [get_ports y]
9
10 ##Buttons
11 set_property -dict { PACKAGE_PIN U18    IOSTANDARD LVCMOS33 } [get_ports rst]
12
13 ## Configuration options, can be used for all designs
14 set_property CONFIG_VOLTAGE 3.3 [current_design]
15 set_property CFGBVS VCCO [current_design]
16
17 ## SPI configuration mode options for QSPI boot, can be used for all designs
18 set_property BITSTREAM.GENERAL.COMPRESS TRUE [current_design]
19 set_property BITSTREAM.CONFIG.CONFIGRATE 33 [current_design]
20 set_property CONFIG_MODE SPIx4 [current_design]
21
```

Snippet from the message after implementation:





Snippet from the utilization after implementation:

Name	1	Slice LUTs (20800)	Slice Registers (41600)	Slice (8150)	LUT as Logic (20800)	LUT Flip Flop Pairs (20800)	Bonded IOB (106)	BUFGCTRL (32)
seq_detector		3	2	1	3	2	4	1

Snippet from the timing after implementation:

Design Timing Summary			
Setup	Hold	Pulse Width	
Worst Negative Slack (WNS): 8.733 ns	Worst Hold Slack (WHS): 0.279 ns	Worst Pulse Width Slack (WPWS): 4.500 ns	
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns	
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	
Total Number of Endpoints: 2	Total Number of Endpoints: 2	Total Number of Endpoints: 3	
All user specified timing constraints are met.			

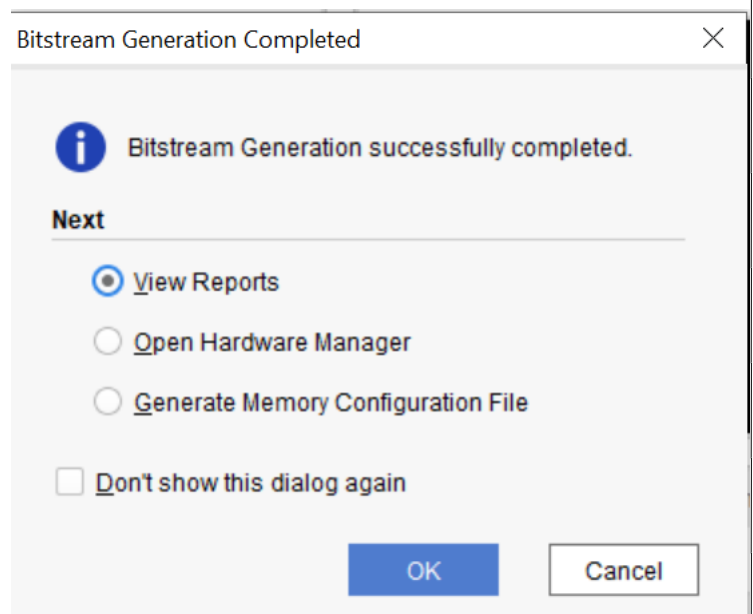 Snippet from the device after implementation:



Q [4]


Code:

```
1  module rom_8x4_sync(clk,rst,addres,data_out);
2
3      input clk,rst;
4      input [2:0]addres ;
5
6      output reg [3:0]data_out;
7
8      always @(posedge clk ) begin
9          if(rst)
10             data_out<=0;
11         else begin
12             case (addres)
13                 0:data_out <= 4'b0001;
14                 1:data_out <= 4'b0010;
15                 2:data_out <= 4'b0100;
16                 3:data_out <= 4'b1000;
17                 4:data_out <= 4'b0001;
18                 5:data_out <= 4'b0010;
19                 6:data_out <= 4'b0100;
20                 7:data_out <= 4'b1000;
21                 default: data_out = 4'b0000;
22             endcase
23         end
24     end
25 endmodule
26
```


Testbench:

```
1 module rom_8x4_sync_tb();
2
3     reg clk_tb,rst_tb;
4     reg [2:0]adres_tb ;
5     reg [3:0]data_out_expect;
6
7     wire [3:0]data_out_dut;
8
9     rom_8x4_sync dut(clk_tb,rst_tb,adres_tb,data_out_dut);
10    initial begin
11        clk_tb=0;
12        forever
13            #1 clk_tb=~clk_tb;
14    end
15    initial begin
16        rst_tb = 1;data_out_expect=0;
17        @(negedge clk_tb);
18        rst_tb =0;
19
20        //read from adres 0
21        adres_tb = 0 ; data_out_expect = 4'b0001;
22        @(negedge clk_tb )
23        if(data_out_dut != data_out_expect)begin
24            $display ("error : data_out_dut = %h,data_out_expect=%h",data_out_dut,data_out_expect);
25            $stop;
26        end
27
28        //read from adres 1
29        adres_tb = 1 ; data_out_expect = 4'b0010;
30        @(negedge clk_tb )
31        if(data_out_dut != data_out_expect)begin
32            $display ("error : data_out_dut = %h,data_out_expect=%h",data_out_dut,data_out_expect);
33            $stop;
34        end
35
36        //read from adres 2
37        adres_tb = 2 ; data_out_expect = 4'b0100;
38        @(negedge clk_tb )
39        if(data_out_dut != data_out_expect)begin
40            $display ("error : data_out_dut = %h,data_out_expect=%h",data_out_dut,data_out_expect);
41            $stop;
42        end
43
44        //read from adres 3
45        adres_tb = 3 ; data_out_expect = 4'b1000;
46        @(negedge clk_tb )
47        if(data_out_dut != data_out_expect)begin
48            $display ("error : data_out_dut = %h,data_out_expect=%h",data_out_dut,data_out_expect);
49            $stop;
50        end
51
52        //read from adres 4
53        adres_tb = 4 ; data_out_expect = 4'b0001;
54        @(negedge clk_tb )
55        if(data_out_dut != data_out_expect)begin
56            $display ("error : data_out_dut = %h,data_out_expect=%h",data_out_dut,data_out_expect);
57            $stop;
58        end
59
60        //read from adres 5
61        adres_tb = 5 ; data_out_expect = 4'b0010;
62        @(negedge clk_tb )
63        if(data_out_dut != data_out_expect)begin
64            $display ("error : data_out_dut = %h,data_out_expect=%h",data_out_dut,data_out_expect);
65            $stop;
66        end
67
68        //read from adres 6
69        adres_tb = 6 ; data_out_expect = 4'b0100;
70        @(negedge clk_tb )
71        if(data_out_dut != data_out_expect)begin
72            $display ("error : data_out_dut = %h,data_out_expect=%h",data_out_dut,data_out_expect);
73            $stop;
74        end
75
76        //read from adres 7
77        adres_tb = 7 ; data_out_expect = 4'b1000;
78        @(negedge clk_tb )
79        if(data_out_dut != data_out_expect)begin
80            $display ("error : data_out_dut = %h,data_out_expect=%h",data_out_dut,data_out_expect);
81            $stop;
82        end
83        $display ("testbench is correct ^_^");
84        $stop;
85    end
86 endmodule
87
```


wave:

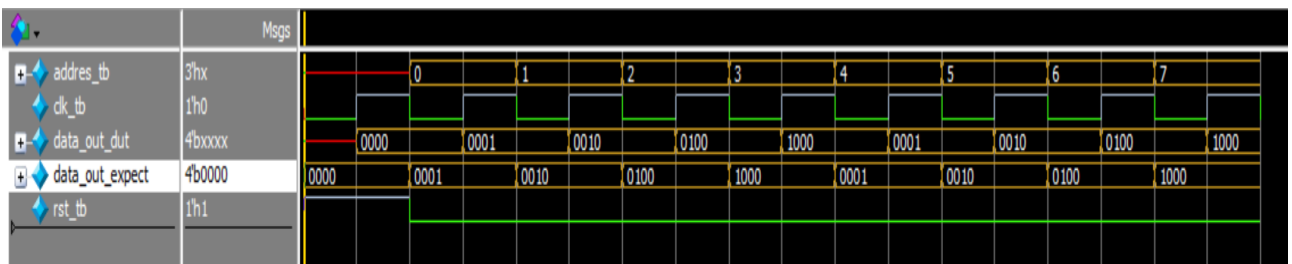

 
Linting snippet free from warnings or errors:



 
Snippets from the schematic after the synthesis:



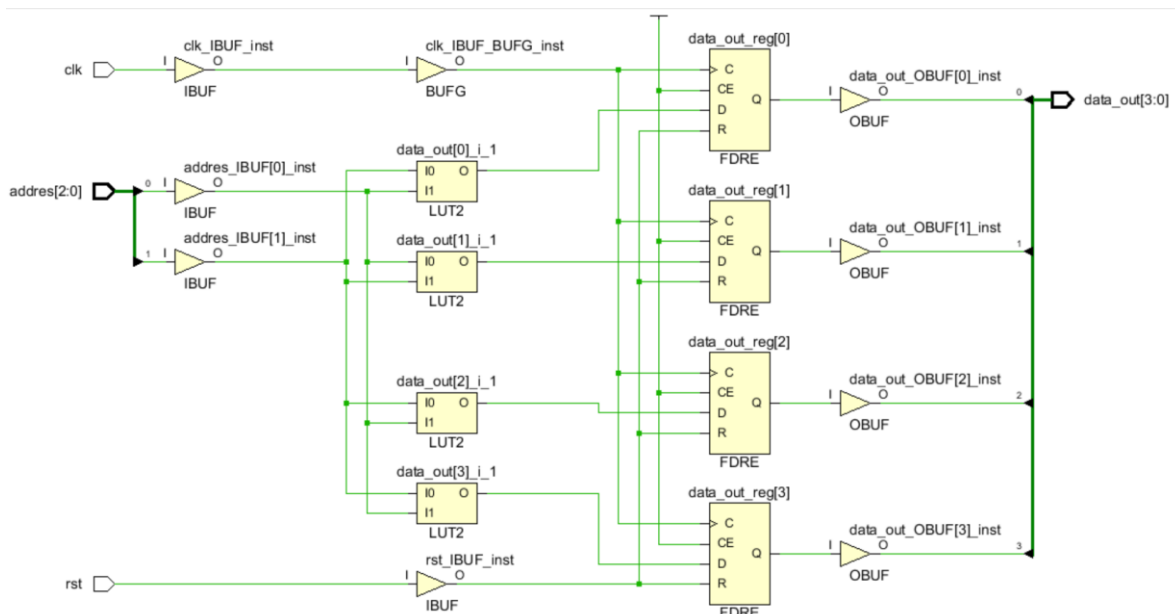Snippets from the schematic after the synthesis:



 Snippet from the device after implementation:



Q [5]

Code:

Verilog code for Assignment 2 Q5 is as follows

```
1 module CRC_detect(clk,reset_n,data_in,data_valid,crc);
2
3     input clk,reset_n,data_in,data_valid;
4
5     output reg [3:0]  crc;
6
7     wire xor_out_1,xor_out_2;
8
9     assign xor_out_1 = data_in^crc[3];
10    assign xor_out_2 = crc[0]^crc[3] ;
11
12    always @(posedge clk or negedge reset_n) begin
13        if(~reset_n)
14            crc<=0;
15        else begin
16            if(data_valid) begin
17                crc[0] <= xor_out_1 ;
18                crc[1] <= xor_out_2 ;
19                crc[2] <= crc[1];
20                crc[3] <= crc[2];
21            end
22        end
23    end
24 endmodule
25
```

Testbench:

```
1  module CRC_detect_tb();
2
3  reg clk,reset_n,data_in,data_valid;
4  wire [3:0]crc_dut;
5  CRC_detect dut (clk,reset_n,data_in,data_valid,crc_dut);
6  initial begin
7      clk = 0;
8      forever
9          #1 clk = ~clk;
10 end
11 initial begin
12     //reset_n
13     reset_n = 0 ; data_valid = 1;
14     @(negedge clk);
15     reset_n = 1 ;
16
17     //insert message.
18     data_in = 1 ; @(negedge clk);
19     data_in = 0 ; @(negedge clk);
20     data_in = 1 ; @(negedge clk);
21     data_in = 1 ; @(negedge clk);
22     data_in = 0 ; @(negedge clk);
23     data_in = 0 ; @(negedge clk);
24     data_in = 1 ; @(negedge clk);
25     data_in = 0 ; @(negedge clk);
26     data_in = 0 ; @(negedge clk);
27     data_in = 0 ; @(negedge clk);
28     data_in = 0 ; @(negedge clk);
29     if (crc_dut != 4'b1010)begin
30         $display("error : crc_dut =%h",crc_dut);
31         $stop ;
32     end
33     $display("testbench is correct ^_^ ");
34     $stop ;
35 end
36 endmodule
```

Wave:

